

The exam has 100 pts. Closed book, no calculators. Write all answers and show all work inside your blue book. Show your work for partial/full credit. **Read carefully.**

Problem 1 (16 pts).

Using several of the 1024x4 RAM chip shown in Figure 1 and any additional combinatorial circuitry (muxes, gates, etc.), implement an equivalent 4096x8 RAM chip. Carefully label your equivalent circuit's write-enable (not), chip-select (not), input/output, and address pins. Indicate MSB and LSB on your address pins.

Problem 2 (4 pts).

Give the truth-table of a tri-state buffer. Describe how tri-state buffers are used internally in RAM chips (such as the chip in Problem 1).

Problem 3 (15pts).

Consider the Mod-N counter in Fig. 2. Assume the circuit starts in the $Q_1Q_0 = 00$ state.

- Is this circuit synchronous or asynchronous? Why?
- Draw a timing diagram to determine the states of the counter. Include glitch-states from propagation delay (if they exist).
- Denote the FF states below your timing diagram in decimal, interpreting Q_1 as the MSB and Q_0 as the LSB.
- What Mod is the counter?

Problem 4 (15pts).

A bidirectional shift-register (BSR) is one in which bits are shifted from left to right ($R = 1$) or right to left ($R = 0$) on the edge of a clock pulse, depending on input R .

- Design a 4-bit BSR with edge-triggered D flip-flops. Your BSR should have a left Data-input D_L , right Data-input D_R , a direction pin R , and parallel output pins $Q_0Q_1Q_2Q_3$. You may use gates and muxes/demuxes in your design.
- Briefly describe how you can augment your design to allow for parallel *loading* of data into the register.

 


Figure 1: RAM chip.

 


Figure 2: Counter circuit.

Problem 5 (20 pts).

In this problem, you will build a synchronous Mod-4 binary up counter which is *both* “pause-able” and “resetable”, i.e. it *pauses counting* when an input signal \overline{P} is low, and *resets to zero* when input signal \overline{R} is low. Otherwise, it continues counting up (with wrap-around). Note that reset should take precedent over pause.

- (a) Construct a state transition diagram for your counter.
- (b) Convert your state transition diagram to a table, labeling current states, inputs, control variables, and next states. Determine values for your control variables to achieve the desired transitions.
- (c) Determine simplified boolean expressions for your control variables.
- (d) Draw a logic diagram of your circuit. Label the clock, \overline{P} , \overline{R} , and your state variables clearly.

Problem 6 (10 pts).

Consider the “pause-able”+“resetable” Mod-4 synchronous circuit constructed in Problem 5.

- (a) Using a single counter from Problem 5, implement a “chain-able”+resetable Mod-4 up-counter, such that the chain-in (C_{in}) pin of a more significant chainable counter could be connected to the chain-out pin (C_{out}) of a less significant chainable counter.
- (b) Implement a Mod-16 synchronous up-counter using your “chain-able”+resetable Mod-4 up-counter(s).

Problem 7 (10 pts).

Consider the “pause-able”+“resetable” Mod-4 synchronous circuit constructed in Problem 5.

- (a) Using a single counter from Problem 5, implement a “pause-able”+“programmable” Mod-4 up-counter, such that given an input 2-bit number $B = B_1B_0$, the counter only reaches a maximum value of B before wrapping around.

Problem 8 (10 pts).

Consider the “pause-able”+“resetable” Mod-4 synchronous circuit constructed in Problem 5.

- (a) Using a single counter from Problem 5, implement a “chain-able”+“programmable” Mod-4 up-counter (see Problems 7 and 8 for descriptions).
- (b) Implement a programmable Mod-16 synchronous up-counter using your “chain-able” + “programmable” Mod-4 up-counter(s), which takes as input a binary number $B = B_3B_2B_1B_0$.